

15

Good!

CSE260

Quiz 3

Name: Maisha Maisara

ID: 23101499

Section: 04

1. Build Excess-5 to BCD converter using Parallel adder. You can use external gates if necessary.


[7 marks]

2. Implement the following function using exactly five 3x8 decoders:

$$F(A,B,C,D,E) = \sum(0,2,3,5,8,11,18,19,23,26,27) \quad 5 \times 32$$

You MUST use logic gates in input/output if required. In the case of logic gates, you may use more than 2 inputs together. Unused input connection(s) should be connected to ground. Mention MSB and LSB accurately.

[8 marks]

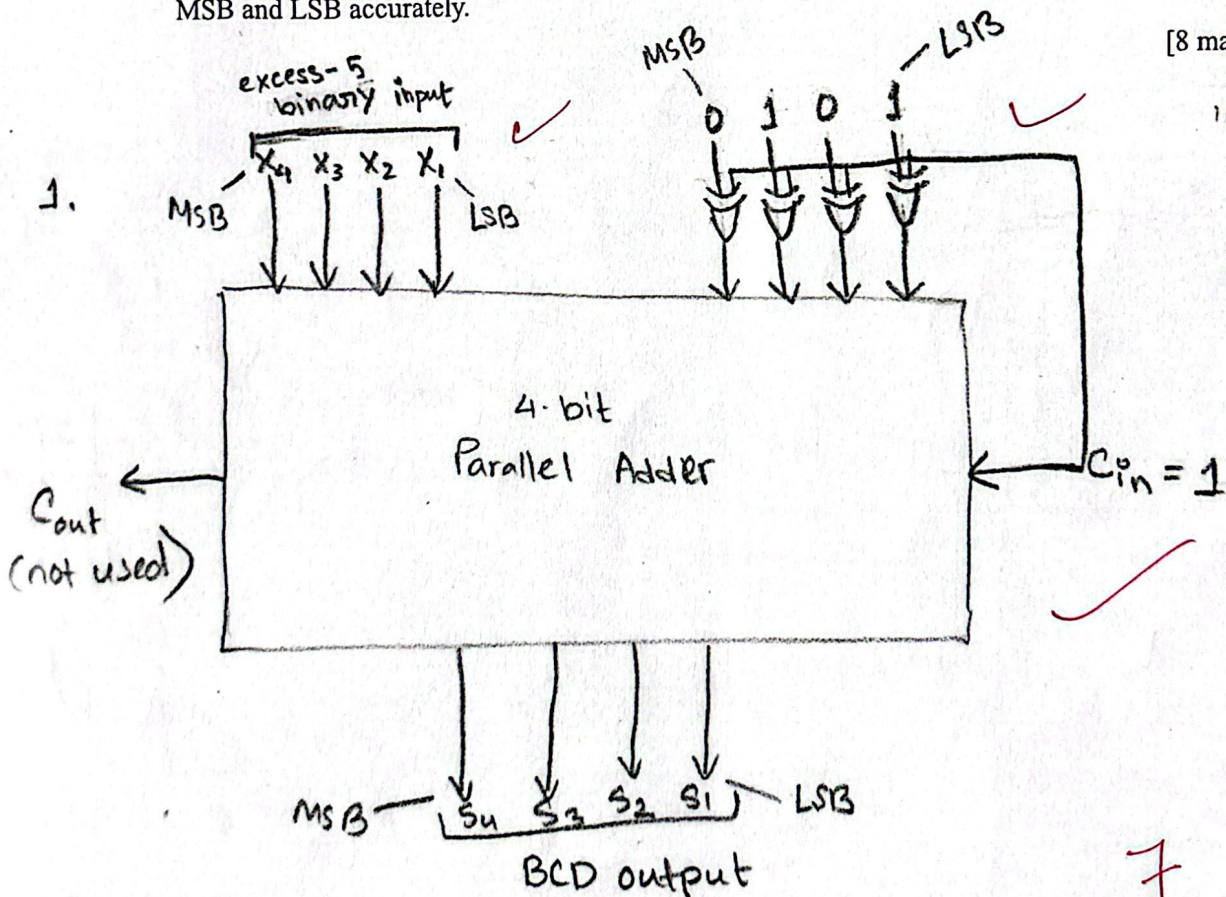

2127
2113
218-1
213-1
211-1
210-1

16 8 4 2 1
0 1 0 1
1 1 0 1 1
1 0 0 0 1

7

MSB A B C D E $\overline{GND}$

11000

2) A B C D E
MSB LSB

