

13.5
15

CSE260
Quiz 3


Name: Saad Abdullah

ID: 22201092

Section: D3

- Construct the function $F(a,b,c,d,e): \sum (3,5,6,11,16,19,22,26,29)$ using 2x4 decoder(s) only. [7 marks]
- Design a circuit diagram for the following system that takes two 4-bit binary numbers [A and B] as inputs and outputs in the following fashion:
 - If one input is odd and the other input is even, the output should be $A-B$
 - If both inputs are odd or both inputs are even, the output should be $A+B$

[8 marks]

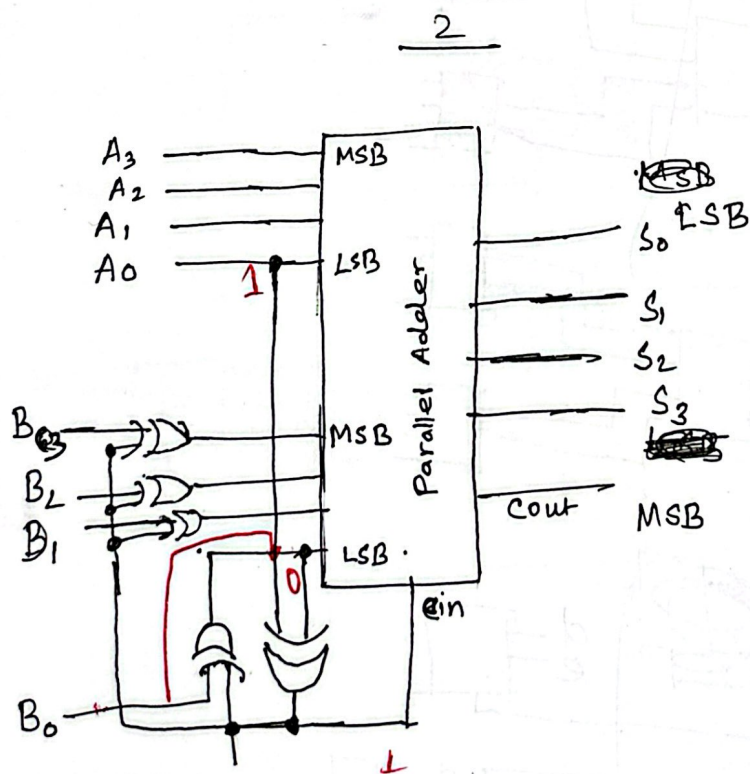


0	0	0
0	0	0
1	0	1
0	1	1
1	1	1

7

Subject:

Date:

10	11	12
----	----	----

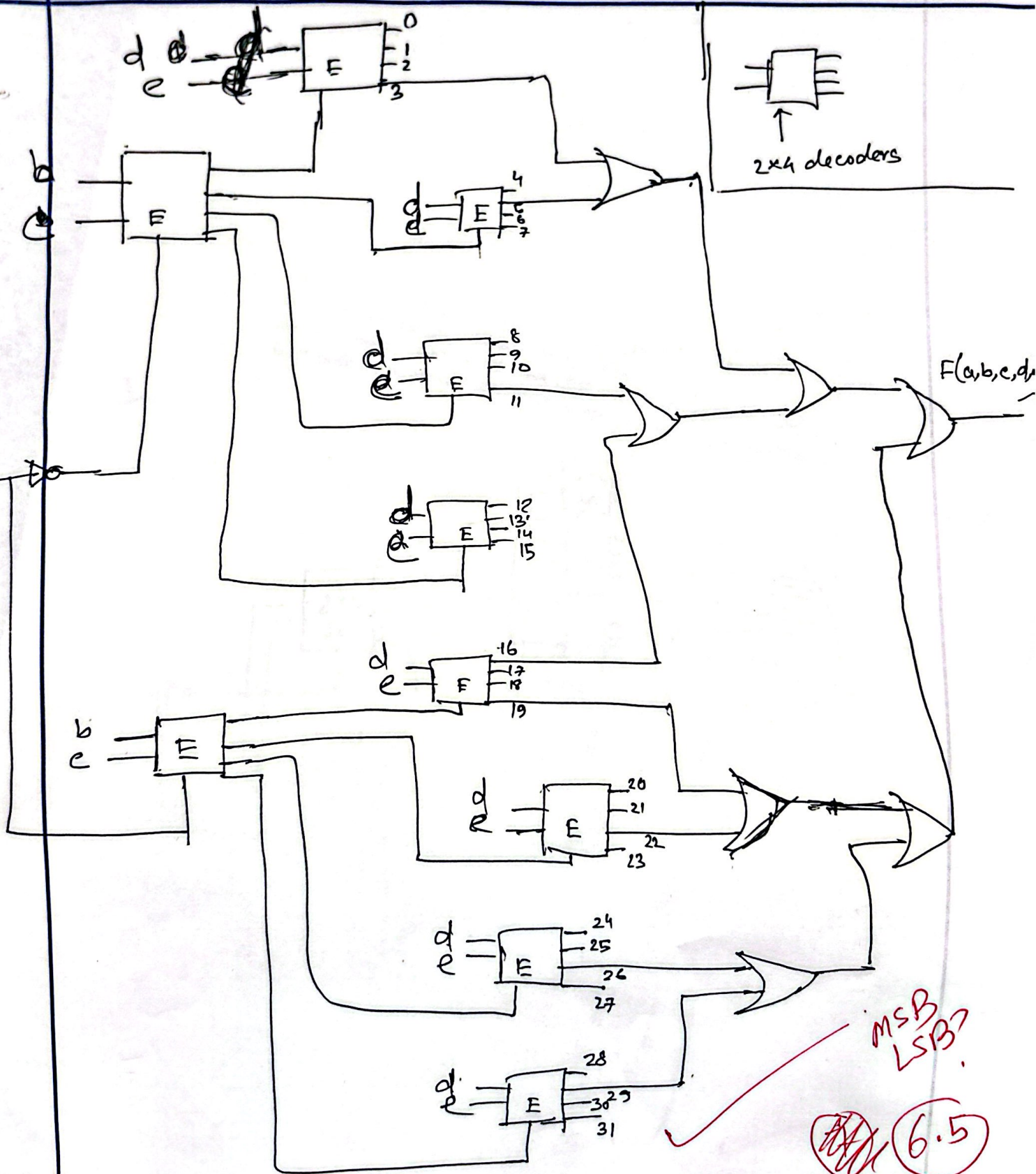

MSB
LSB?

6.5