

[Assignment-4]

Name: Imtiaz Hossain


ID : 23101137

Section: 1

Course : CSE 260
code :

Faculty : [REDACTED] [FIC]
Initial :

Ans to the Q. No : 2

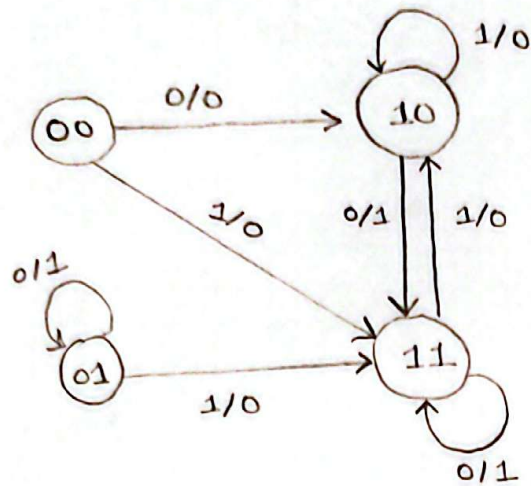

A_1	A_0	X	A_1^+	A_0^+	Y	JA_1	KA_1	JA_0	KA_0
0	0	0	1	0	0	1	X	0	X
0	0	1	1	1	0	1	X	1	X
0	1	0	0	1	1	0	X	X	0
0	1	1	1	1	0	1	X	X	0
1	0	0	1	1	1	X	0	1	X
1	0	1	1	0	0	X	0	0	X
1	1	0	1	1	1	X	0	X	0
1	1	1	1	0	0	X	0	X	1

K-MAP: For Y ,

$A_1 \backslash A_0 X$	$A_0' X'$	$A_0' X$	$A_0 X$	$A_0 X'$
A_1'	0	1	3	1
A_1	4	5	X	6

Excitation Table

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$$\begin{aligned}
 Y &= A_0 X' + A_1 X' \\
 &= X' (A_0 + A_1)
 \end{aligned}$$

