
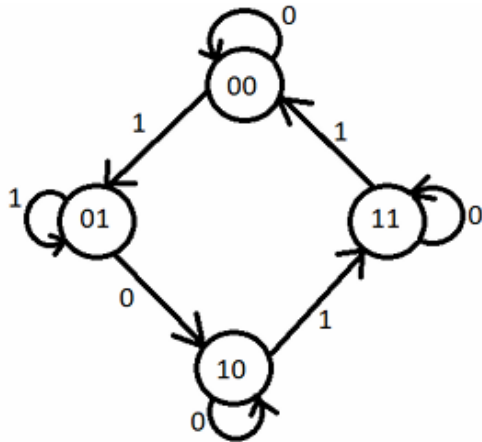


Assignment 4

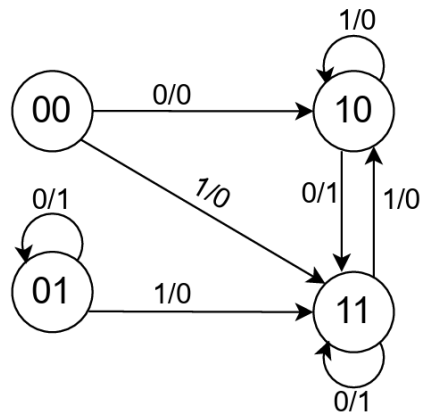1. Given the state diagram as follows, get the sequential circuit using SR flipflop.
(Ungraded)



2. Given the state diagram as follows, get the sequential circuit using JK flipflop.
(Graded)



3. Draw the state diagram for the given circuit. (Ungraded)

